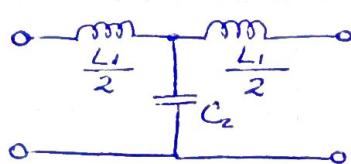


$$\begin{aligned} Z_1^2 + 2 \cdot 20 \cdot Z_1 - 50^2 &= 0 \\ Z_1^2 + 40Z_1 - 2500 &= 0 \end{aligned} \quad \left\{ \begin{array}{l} (Z_1)_1 = 33,851 \Omega \\ (Z_1)_2 = -73,851 \Omega \end{array} \right.$$

$$Z_1 = Z_3 = 33,851 \Omega$$

107) Calcular los componentes de un filtro pasa-bajos Kote considerando  $R_o = 600 \Omega$  y  $f_c = 3 \text{ kHz}$ .




$$L_1 = \frac{2R_o}{\omega_c} \rightarrow \frac{L_1}{2} = \frac{R_o}{\omega_c}$$


$$C_2 = \frac{2}{R_o \omega_c}$$

$$\frac{L_1}{2} = \frac{600}{2\pi \cdot 3 \times 10^3} \text{ H} \Rightarrow 31,83 \text{ mH.} = \frac{L_1}{2}$$

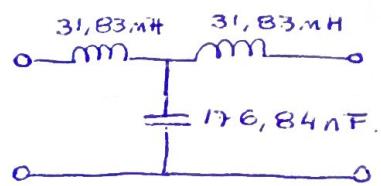
$$C_2 = \frac{2}{600 \times 2\pi \cdot 3 \times 10^3} = 176,84 \text{ nF} = C_2$$




Simulación NI Multisim 14.1.

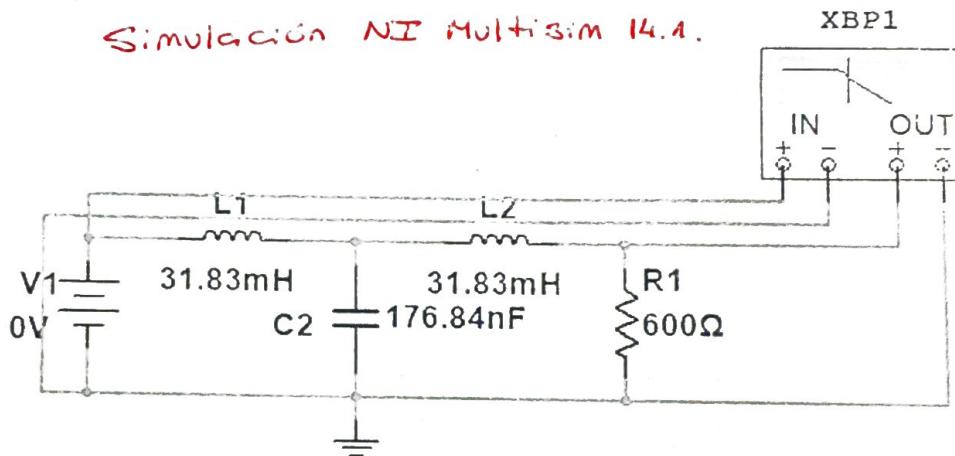

XBP1

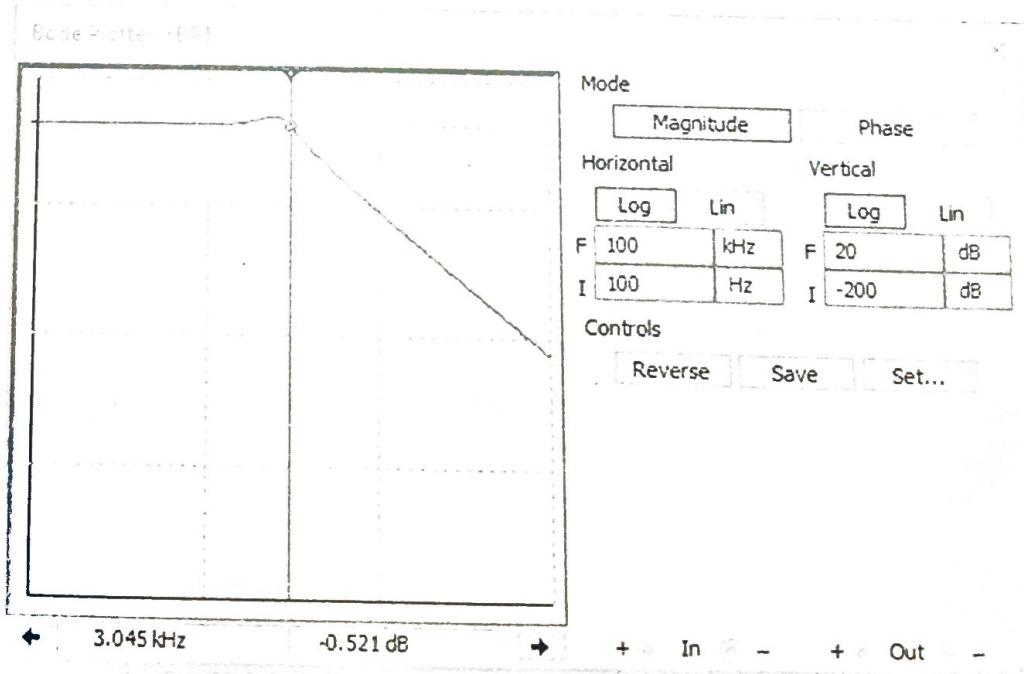

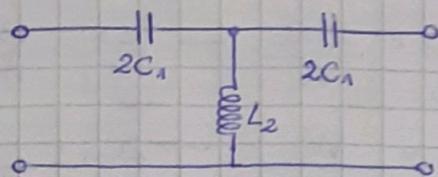108) Calcular los componentes de un filtro pasa-altos Kote considerando  $R_o = 600\Omega$  y  $f_c = 3\text{kHz}$ .



$$C_1 = \frac{1}{2R_o W_c} \rightarrow 2C_1 = \frac{1}{R_o W_c}$$


$$L_2 = \frac{R_o}{2W_c}$$

$$2C_1 = \frac{1}{600 \times 2\pi \times 3 \times 10^3} F = 88,42\text{nF}$$



$$L_2 = \frac{600}{2 \times 2\pi \times 3 \times 10^3} H = 15,91\text{mH}$$

$$2C_1 = 88,42\text{nF}$$


$$L_2 = 15,91\text{mH}$$

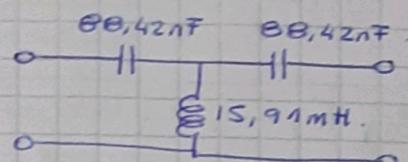


Simulación NI Multisim 14.1.

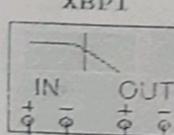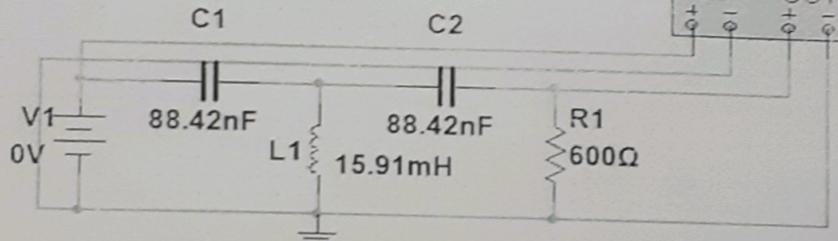

Bode Plotter-XBP1

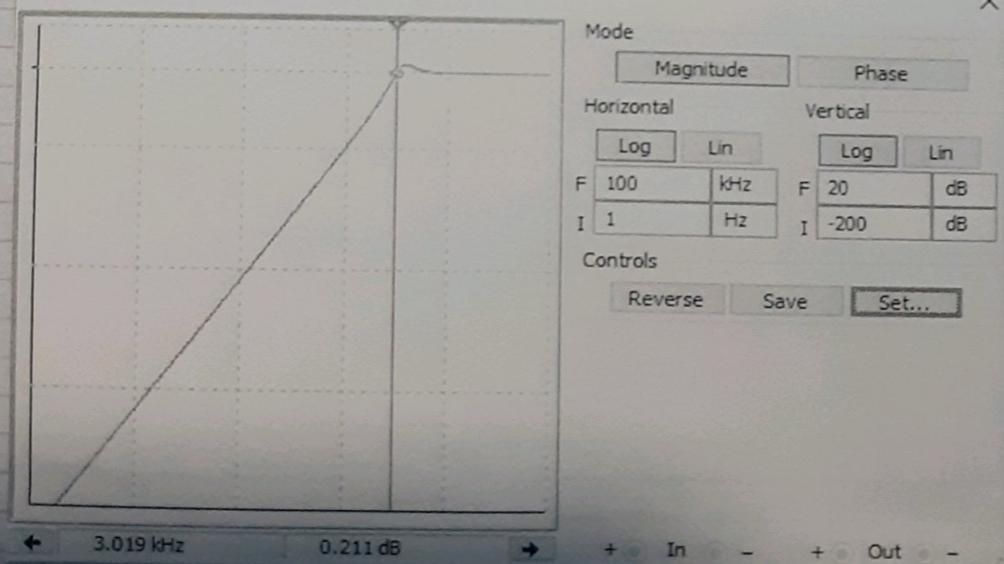

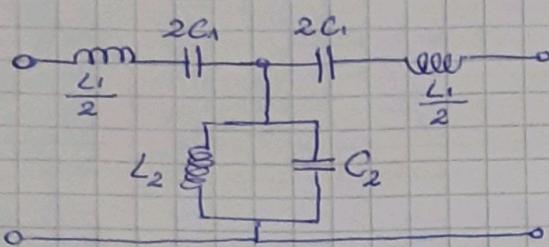109) Calcular los componentes de un filtro pasa-banda kde considerando  $R_o = 600\Omega$ , con  $f_{c1}$  (inferior) = 1 kHz y  $f_{c2}$  (superior) = 4 kHz.



$$F(\text{Ancho de banda}) = f_{c2} - f_{c1} = 3 \text{ kHz}$$

$$W = 2\pi \cdot F = 2\pi \cdot 3 \times 10^3 \text{ rps}$$

$$L_1 = \frac{2R_o}{W} \rightarrow \frac{L_1}{2} = \frac{R_o}{W}$$

$$C_1 = \frac{W}{2R_o W_0^2} \rightarrow 2C_1 = \frac{W}{R_o \cdot W_0^2}$$

$$L_2 = \frac{R_o}{2W}$$

$$C_2 = \frac{2W}{R_o W_0^2}$$

$W_0 \rightarrow$  media geométrica entre  $W_{c1}$  y  $W_{c2}$

$$f_0 = \sqrt{f_{c1} \cdot f_{c2}} = \sqrt{1 \text{ kHz} \cdot 4 \text{ kHz}} = 2 \text{ kHz}$$


$$W_0 = 2\pi \cdot 2 \times 10^3 \text{ rps}$$

$$\bullet \frac{L_1}{2} = \frac{600}{2\pi \cdot 3 \times 10^3} \text{ H} = 31,83 \text{ mH} = \frac{L_1}{2}$$


$$\bullet 2C_1 = \frac{2\pi \cdot 3 \times 10^3}{600 \times (2\pi \cdot 2 \times 10^3)} F = 198,94 \text{ nF} = 2C_1$$

$$\bullet L_2 = \frac{600}{2 \cdot 2\pi \cdot 3 \times 10^3} \text{ H} = 15,91 \text{ mH} = L_2$$
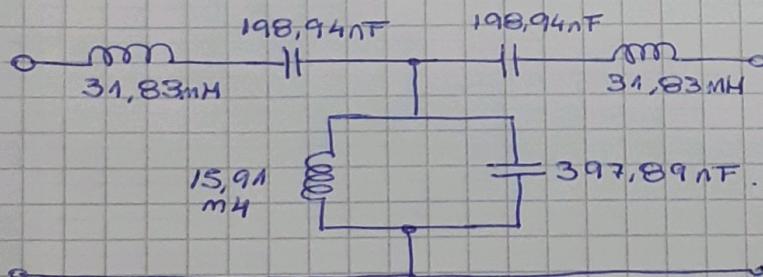
$$\bullet C_2 = \frac{2 \cdot 2\pi \cdot 3 \times 10^3}{600 \cdot (2\pi \cdot 2 \times 10^3)^2} F = 397,89 \text{ nF} = C_2$$



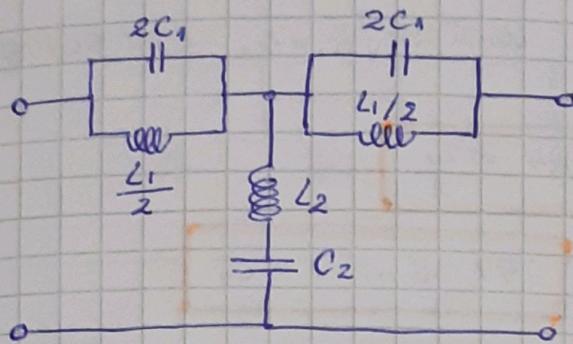110) Calcular los componentes de un filtro elimina-banda kate considerando  $R_o = 600\Omega$ , con  $f_{c1} = 1\text{kHz}$  y  $f_{c2} = 4\text{kHz}$



$$\cdot W = 2\pi (f_{c2} - f_{c1}) = 2\pi \cdot 3 \times 10^3 \text{ rps}$$

$$\cdot \omega_0 = 2\pi \sqrt{f_{c1} \cdot f_{c2}} = 2\pi \cdot 2 \times 10^3 \text{ rps}$$

$$\cdot L_1 = \frac{2 R_o \cdot W}{\omega_0^2} \rightarrow \frac{L_1}{2} = \frac{R_o W}{\omega_0^2}$$

$$\cdot C_1 = \frac{1}{2 R_o W} \rightarrow 2C_1 = \frac{1}{R_o W}$$

$$\cdot L_2 = \frac{R_o}{2 W}$$


$$\cdot C_2 = \frac{2 W}{R_o \omega_0^2}$$

$$\cdot \frac{L_1}{2} = \frac{600 \cdot 2\pi \cdot 3 \times 10^3}{(2\pi \cdot 2 \times 10^3)^2} H = 71,62\text{mH} = \frac{L_1}{2}$$

$$\cdot 2C_1 = \frac{1}{600 \cdot 2\pi \cdot 3 \times 10^3} F = 88,42\text{nF} = 2C_1$$


$$\cdot L_2 = \frac{600}{2 \cdot 2\pi \cdot 3 \times 10^3} H = 15,91\text{mH} = L_2$$
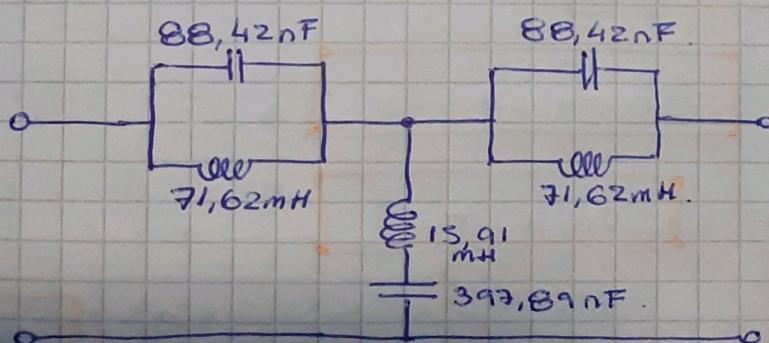
$$\cdot C_2 = \frac{2 W}{R_o \omega_0^2} = \frac{2 \cdot 2\pi \cdot 3 \times 10^3}{600 \cdot (2\pi \cdot 2 \times 10^3)^2} = 397,89\text{nF} = C_2$$



III) Calcular los componentes de un filtro pasa-banda Kote y su m-derivado, con  $R_o = 8 \Omega$  y  $m = 0,6$ , con  $f_{c1} = 8 \text{ kHz}$  y  $f_{c2} = 10 \text{ kHz}$ .

Kote:

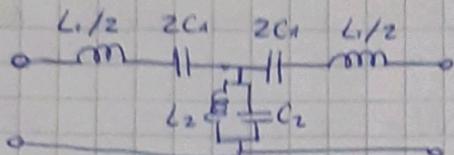

$$W = 2\pi(f_{c2} - f_{c1}) = 2\pi \cdot 2 \cdot 10^3 \text{ rps.}$$

$$W_0 = 2\pi \sqrt{f_{c1} \cdot f_{c2}} \approx 2\pi \cdot 56198,518 \text{ rps}$$



$$\frac{L_1}{2} = \frac{R_o}{W} = \frac{8}{2\pi \cdot 2 \cdot 10^3} H = 636,62 \text{ mH} = \frac{L_1}{2}$$

$$2C_1 = \frac{W}{R_o W_0^2} = \frac{2\pi \cdot 2 \cdot 10^3}{8 \cdot (56198,518)^2} F = 497,36 \text{ nF} = 2C_1$$

$$L_2 = \frac{R_o}{2W} = \frac{8}{2 \cdot 2\pi \cdot 2 \cdot 10^3} H = 318,31 \text{ mH} = L_2$$

$$C_2 = \frac{2W}{R_o W_0^2} = \frac{2 \cdot 2\pi \cdot 2 \cdot 10^3}{8 \cdot (56198,518)^2} = 994,72 \text{ nF} = C_2$$

m-deriv:

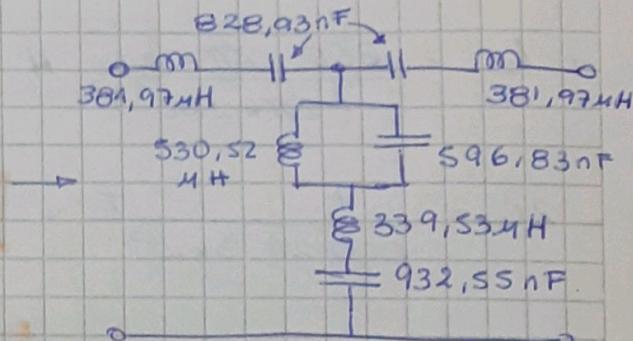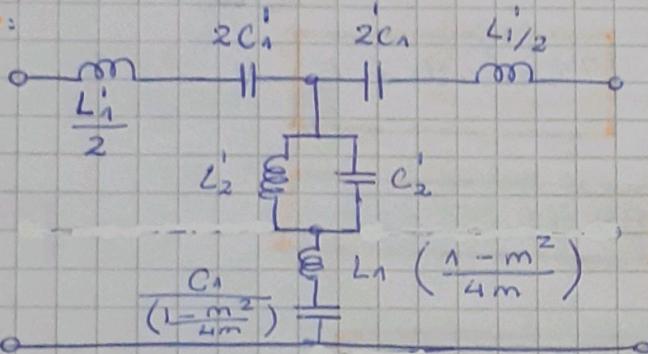

$$\frac{L_1'}{2} = \frac{L_1}{2} \cdot m = 0,6 \times 636,62 \text{ mH} = 381,97 \text{ mH} = \frac{L_1'}{2}$$

$$2C_1' = \frac{2C_1}{m} = \frac{497,36 \text{ nF}}{0,6} = 828,93 \text{ nF} = 2C_1'$$


$$L_2' = \frac{L_2}{m} = \frac{318,31 \text{ mH}}{0,6} = 530,52 \text{ mH} = L_2'$$

$$C_2' = m \cdot C_2 = 0,6 \times 994,72 \text{ nF} = 596,83 \text{ nF} = C_2'$$

$$L_1 \left( \frac{1-m^2}{4m} \right) = \frac{L_1}{2} \left( \frac{1-m^2}{2m} \right) = 636,62 \text{ mH} \left( \frac{1-0,6^2}{2 \cdot 0,6} \right) = 339,53 \text{ mH}$$

$$\frac{C_1}{\left( \frac{1-m^2}{4m} \right)} = \frac{2C_1}{\left( \frac{1-m^2}{2m} \right)} = \frac{497,36 \text{ nF}}{\left( \frac{1-0,6^2}{2 \cdot 0,6} \right)} = 932,55 \text{ nF}$$

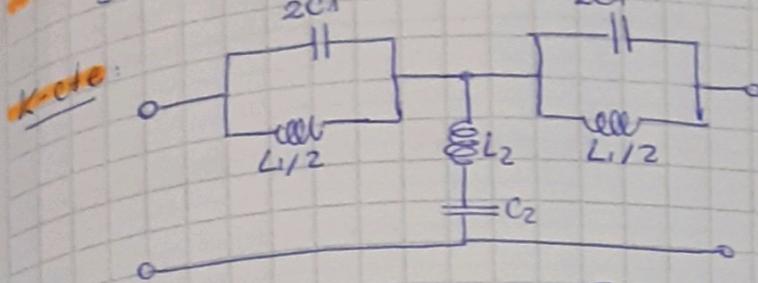112) Calcular los componentes de un filtro eliminabanda Kote y su m-derivado, con  $R_o = 8 \Omega$  y  $m = 0,6$ .  $f_{C_1} = 6 \text{ kHz}$  y  $f_{C_2} = 9 \text{ kHz}$ .





$$\begin{aligned} W &= 2\pi (f_{C_2} - f_{C_1}) = 2\pi \cdot 3 \times 10^3 \text{ cps} \\ W_0 &= 2\pi \sqrt{f_{C_1} \cdot f_{C_2}} = 46171,79 \text{ cps} \end{aligned}$$

$$\frac{L_1}{2} = \frac{R_o W}{W_0^2} = \frac{8 \cdot 2\pi \cdot 3 \times 10^3}{(46171,79)^2} = 70,73 \mu\text{H} = \frac{L_1}{2}$$

$$2C_1 = \frac{1}{R_o W} = \frac{1}{8 \cdot 2\pi \cdot 3 \times 10^3} = 6,63 \mu\text{F} = 2C_1$$

$$L_2 = \frac{R_o}{2W} = \frac{8}{2 \cdot 2\pi \cdot 3 \times 10^3} = 212,21 \mu\text{H} = L_2$$
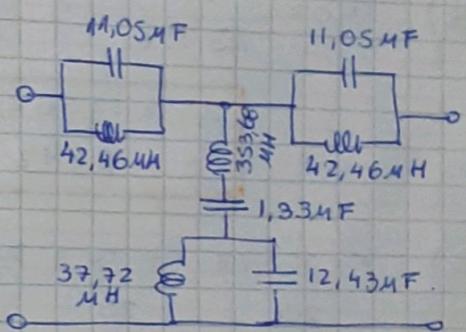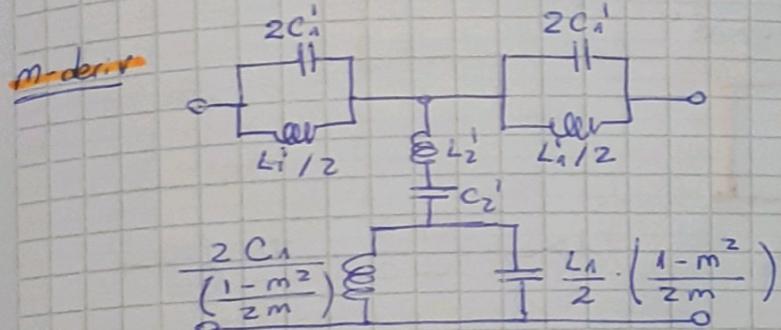
$$C_2 = \frac{2W}{R_o W_0^2} = \frac{2 \cdot 2\pi \cdot 3 \times 10^3}{8 \cdot (46171,79)^2} = 2,21 \mu\text{F} = C_2$$



$$\frac{L_1'}{2} = \frac{L_1 \cdot m}{2} = 0,6 \times 70,73 \mu\text{H} = 42,46 \mu\text{H} = \frac{L_1'}{2}$$

$$2C_1' = \frac{2C_1}{m} = \frac{6,63 \mu\text{F}}{0,6} = 11,05 \mu\text{F} = 2C_1'$$

$$\frac{L_2'}{2} = \frac{L_2 \cdot m}{2} = \frac{212,21 \mu\text{H}}{0,6} = 353,68 \mu\text{H} = L_2'$$


$$C_2' = m C_2 = 0,6 \times 2,21 \mu\text{F} = 1,33 \mu\text{F} = C_2'$$

$$\frac{L_1}{2} \left( \frac{1-m^2}{2m} \right) = 70,73 \mu\text{H} \left( \frac{1-0,6^2}{2 \cdot 0,6} \right) = 37,72 \mu\text{H} =$$

$$\frac{2C_1}{\left( \frac{1-m^2}{2m} \right)} = \frac{6,63 \mu\text{F}}{\left( \frac{1-0,6^2}{2 \cdot 0,6} \right)} = 12,43 \mu\text{F}$$

113) Dado el cuadripolo. Determinar.

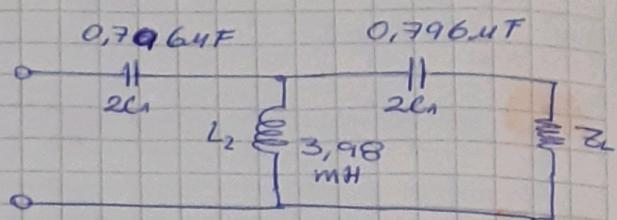- a) Tipo de filtro
- b) Valor de  $Z_0$  (imp. carac.)
- c) Valor de  $Z_L$
- d)  $\omega_c$  (frec de corte)
- e) Atenuación para  $f = 500\text{Hz}$ .



a) Filtro pasa alto.

b) c)  $Z_0 = Z_L = R_0$

$$2C_1 = \frac{1}{R_0 \omega_c} \rightarrow \omega_c = \frac{1}{R_0 2C_1}$$

$$L_2 = \frac{R_0}{2\omega_c} = \frac{R_0}{2\left(\frac{1}{R_0 2C_1}\right)} = \frac{R_0^2 2C_1}{2}$$

$$R_0 = \sqrt{\frac{2L_2}{2C_1}} = \sqrt{\frac{2 \times 3.98 \times 10^{-3}}{0.796 \times 10^{-6}}} \Omega = 100 \Omega$$


$R_0 = 100 \Omega \approx Z_0$

d)  $\omega_c = \frac{1}{R_0 2C_1} = \frac{1}{100 \cdot 0.796 \times 10^{-6}}$

$\omega_c = 12562,81 \text{ rps}$

$f_c = 2 \text{ kHz}$

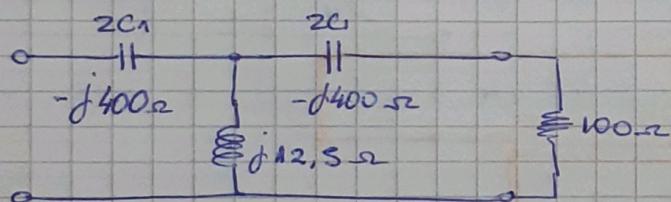e)  $f = 500\text{Hz} \rightarrow \omega = 2\pi \cdot 500\text{Hz}$ . ;  $-jX_C = -\frac{j}{\omega C}$ ;  $jX_L = j\omega L$



\*  $\frac{E_{in}}{E_{out}} = A + \frac{B}{Z_{out}}$

•  $A = \frac{Z_{11}}{Z_{22}} = \frac{-j12,5 - j400}{-j12,5} = -31$

•  $B = \frac{\Delta Z}{Z_{21}} = \frac{(-j400 + j12,5)^2 - (j12,5)^2}{j12,5} = 12000j$


\*  $\frac{E_{in}}{E_{out}} = -31 + \frac{12000j}{100} = 123,94 \angle 104,48^\circ \rightarrow$

$e^\alpha = 123,94 \begin{pmatrix} 4,82 \text{ NP} \\ 41,86 \text{ dB} \end{pmatrix}$

$\beta = 104,48^\circ$

114) Dado el sig. cuad. determinar:

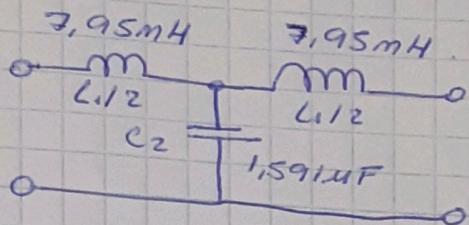- a) T.p. de filtro
- b)  $Z_0$
- c)  $Z_L$
- d)  $\omega_c$
- e) Atenuación para  $f = 3000\text{Hz}$



a) Filtro pasa bajo

b), c)  $Z_0 = Z_L = R_0$ .

$$\frac{L_1}{2} = \frac{R_0}{\omega_c} \quad ; \quad C_2 = \frac{2}{R_0 \omega_c} \rightarrow \omega_c = \frac{2}{C_2 R_0}$$


$$\frac{L_1}{2} = R_0 \cdot \frac{C_2 R_0}{2} \rightarrow R_0 = \sqrt{\frac{L_1/2}{C_2/2}} = \sqrt{\frac{7.95 \times 10^{-3}}{1.591 \times 10^{-6}}} = 100 \Omega$$

$Z_0 = 100 \Omega$

d)  $\omega_c = \frac{2}{C_2 R_0} = \frac{2}{1.591 \times 10^{-6} \times 100} = 12570,71 \text{ rps}$

$\omega_c = 12570,71 \text{ rps}$   
 $f_c = 2 \text{ kHz}$

e) P/3kHz:

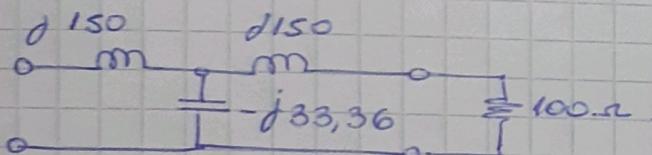

$$\frac{E_{in}}{E_{out}} = A + \frac{B}{Z_{out}}$$

$$A = \frac{j150 - j33,36}{j33,36} = 3,5$$

$$B = \frac{(j150 - j33,36)^2 - (-j33,36)^2}{-j33,36} = -j374,46$$

$$\frac{E_{in}}{E_{out}} = 3,5 - j \frac{374,46}{100} = 5,12 \angle -46,93^\circ$$

$e^{\alpha} = 5,12 \quad \left( \begin{array}{l} 1,63 \text{ NP} \\ 14,18 \text{ dB} \end{array} \right)$   
 $\beta = -46,93^\circ$